#### 6- Passive and Active RF Lumped Components

The information in this work has been obtained from sources believed to be reliable. The author does not guarantee the accuracy or completeness of any information presented herein, and shall not be responsible for any errors, omissions or damages as a result of the use of this information.

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### References

- [1] Ludwig R., Bretchko P., "RF circuit design theory and applications", 2000, Prentice Hall.
- [2] Laverghetta T.S., "Practical Microwaves", 1996, Prentice-Hall.
- [3] Robertson I. D., Lucyszyn S. (Editors), "RFIC and MMIC design and technology", 2001, IEE Circuits, Devices and Systems Series 13.
- [4] Gray P. R., Meyer R. G., "Analysis and design of analog intergrated circuits", 3rd Edition, 1993, John-Wiley & Sons. Note: 5<sup>th</sup> (2009) edition of this book is available with newer materials.
- [5] Millman J., Halkias C. C., "Integrated electronics", 1972, McGraw-Hill.
- [6] Massobrio G., Antognetti P., "Semiconductor device modeling with SPICE", 2nd edition 1993, McGraw-Hill.
- [7] Sze S. M., "Semiconductor devices physics and technology", 3<sup>rd</sup> edition 2012, John-Wiley & Sons.
- [8] Gilmore R., Besser L.,"Practical RF circuit design for modern wireless systems", Vol. 1 & 2, 2003, Artech House.
- [9]\* D.M. Pozar, "Microwave engineering", 4th Edition, 2011 John-Wiley & Sons.

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### **Agenda**

- Passive lumped components at RF.
- · Surface-mounted packaging.
- A review of bipolar junction transistor (BJT) operation and model.
- · Overview of other active RF components.
- · Biasing circuit design for BJT and basic amplifier circuit.
- Frequency response for basic amplifier circuit (S-parameters).
- Appendix examples of active RF circuits.

Chapter 6 (November 2016)


© 2012-2016 by Fabian Kung Wai Lee

# 1.0 Lumped Components at Radio Frequency (RF)

Chapter 6 (November 2016)


© 2012-2016 by Fabian Kung Wai Lee
 
# Passive Lumped Components for Medium Frequency (up to 300MHz)


 
#### **Effect of Packaging**

- How the component is packaged is very important at high frequencies.
- When a component is energized (e.g. voltage and current applied):



 To reduce unwanted lead inductance and capacitance, a smaller package size with shorter leads is preferred. This results in the birth of surface-mounted technologies (SMT). SMT also enable miniaturization of the physical circuits.

Chapter 6 (November 2016)


© 2012-2016 by Fabian Kung Wai Lee

 $\epsilon$ 
 
#### **Passive Lumped Components at RF (1)**

- At radio frequencies a component is not what it appears to be.
- · For instance consider a resistor in leaded package:

Note: Make sure you understand the meaning of 'lumped', and its opposite, the 'distributed'.



A more accurate representation would be:


ccurate representation would be: 
$$Z_{practical}(\omega) = j\omega L_{lead} + \left(\frac{R}{1 + j\omega RC_p}\right)$$

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee
 
#### **Passive Lumped Components at RF (2)**

• The magnitude and phase of the resistor's impedance as a function of frequency:




Only in this range will the component


behave as an ideal resistor, usually f<sub>res</sub> is < 250MHz for leaded resistors

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

• 4

 


 
 
#### **Surface-Mounted Package**

- Surface-mount technology (SMT) was developed in the 1960s and became widely used in the late 1980s. Much of the pioneering work in this technology was done at the then IBM.
- Instead of leads, components were mechanically redesigned to have small metal tabs or end caps to be directly soldered to the surface of the PCB.

Components became much smaller. Elimination of leads also reduces parasitic inductance and capacitance or the component, allowing apparation at higher frequency.





#### **Who Determines the Package Dimension?**


- A package dimension and style is usually determined by the needs of the electronic industry.
- Usually a dominant component manufacturing company will introduce a new package type based on current needs. The mechanical design will be proposed to a standard making body.
- If sufficient players adopt the package, it will become an accepted standard and a formal document is drafted to describe its characteristics.
- At present in North America the standards for SMT and other components is drafted by the JEDEC Solid State Technology Association (JEDEC - Joint Electron Device Engineering Council), <a href="http://www.jedec.org/">http://www.jedec.org/</a>. JEDEC members consist of electronics and semiconductor companies worldwide.
- JEDEC also works closely with Electronic Industries Association of Japan (EIAJ) to focus on similar package outlines from each organization into one world-wide standard package outline.


Chapter 6 (November 2016)


© 2012-2016 by Fabian Kung Wai Lee

 


 


 

 

 

 

 



#### **RF BJT Construction (1)**


- Almost all RF transistors are NPN, because mobility of electron is much higher than hole in Silicon ( $\mu_e$  = 0.13m<sup>2</sup>V<sup>-1</sup>s<sup>-1</sup>,  $\mu_h$  = 0.05m<sup>2</sup>V<sup>-1</sup>s<sup>-1</sup>). The mobility is inversely proportional to the base transit time,  $\tau$ .
- The **Base** thickness is very thin, to improve current gain  $h_{fe}$  at high frequencies. The  $h_{fe}$  is related to a parameter known as base transit time  $\tau$ , smaller  $\tau$  yields larger  $h_{fe}$ .
- Inter-digital Base and Emitter contacts are employed to reduce base spreading resistance r<sub>b'b</sub> and to reduce the noise generated by the transistor.
- The base transit time  $\tau$  can be reduced further if electrons are accelerated across the base by electric field (E). This is achieved by deliberately introducing doping concentration profile in the base.
- Low-cost commercial RF transistors in discrete form can have f<sub>T</sub> up to 10 GHz. Examples of RF BJT are BFR92A (f<sub>T</sub> = 5 GHz) and BFG520 (f<sub>T</sub> = 9 GHz), from NXP Semiconductors (www.nxp.com) and Infineon Technologies.

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

 

 

 

#### The Parameters of Hybrid-Pi Model (1)

- The names of the various parameters:
  - r<sub>bb</sub>, Base spreading resistance (also given as r<sub>x</sub>)
  - g<sub>m</sub> Transconductance (it relates voltage to current)
  - C<sub>e</sub> Emitter capacitance
  - C<sub>c</sub> Collector capacitance
  - $r_{b^{\prime}c}$  Collector to base resistance (also given as  $r_{\mu})$
  - $r_{b'e}$  Base to emitter resistance (also given as  $r_{\pi}$ )
  - r<sub>ce</sub> Output resistance (also given as r<sub>o</sub>)

Alternatively see the proof by F. Kung on how to get the hybrid-Pi model of a BJT using Taylor Series Expansion of the V-I relationship of BE and BC junctions, March 2000.

The Hybrid-Pi model is a fairly accurate description of the BJT small-signal response up to GHz frequency range. You can find more information on the Hybrid-Pi model in [4].

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### The Parameters of Hybrid-Pi Model (2)

#### Physical explanation of the Hybrid-Pi parameters...

r <sub>bb</sub> ,	The base-spreading resistance - The base region is very thin. Current, which					
	enters the base region across the emitter junction, must flow through a long					
	narrow path to reach the base terminal. Hence the ohmic resistance of the base					
	is very much larger than that of the collector or emitter. The manufacturer of					
	the transistor usually provides this value.					
$g_{\rm m}$	The transconductance – The transconductance is defined as:					
	$g_m = \frac{dI_C}{dV_{BE}} = \frac{qI_C}{kT} \approx \frac{I_C (\text{in mA})}{26}$ at T=25°, q= electronic charge, 1.602x10 <sup>-19</sup> C					
	Where $I_C$ is the dc collector current.					
Ce	The emitter capacitance - Ce represents the sum of the emitter diffusion					
	capacitance C <sub>DE</sub> (or base charging capacitance) and the emitter junction					
	depletion region capacitance C <sub>TE</sub> .					
	$C_e = C_{DE} + C_{TE}$					
	$C_{DE}$ is due to finite charge transit time in the emitter PN junction, it is given by Gray & Meyer [4], chapter 1 and Millman & Halkias [5], chapter 11 as:					
	$C_{DE} = \tau_F g_m$					
	Where $\tau_F$ = forward baised base transit time.					
	The depletion region capacitance depends on the biasing voltage across the PN					
	junction and the doping profile of the junction. The expression is rathe					
	lengthy, the interested reader can consult Gray & Meyer [4], chapter 1.					

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

2

#### The Parameters of Hybrid-Pi Model (3)

#### The input resistance – This resistance is defined by Gray & Meyer [4],

	chapter 1:
	$r_{b^{\prime}e}=rac{dV_{B^{\prime}E}}{dI_{B}}=rac{h_{fe}}{g_{m}}$
r <sub>b'c</sub>	The collector to base resistance – In active region, the collector junction of a transistor is reverse biased. Hence when V <sub>CE</sub> changes, the depletion region
	width of the collector junction also changes, this modulates the effective length of the base and a change in total minority carrier charge $Q_m$ stored in the base.
	$I_C$ is a function of $Q_m$ , consequently the collector current also changes. This effect is modeled by the inclusion of $r_{b^*c}$ .
	$r_{b'c} = h_{fe}r_{ce}$
	Usually $r_{b'c} >> r_{b'e}$ and can be ignored.
$C_{C}$	The collector capacitance – C <sub>C</sub> is the depletion region capacitance between
	the collector and base PN junction. It is important as Miller effect can greatly
	increases its effect.

The output resistance – The output resistance is due to base-width modulation effect or the Early effect. It is given by (Gray & Meyer [4], chapter 1):

 $r_{ce} = \frac{V_A}{I_C} = \frac{qV_A}{kTg_m}$ 

Where  $V_A$  is known as the Early voltage and  $I_C$  is the dc collector current.

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee



#### Validity of the Hybrid - Pi Model

• The Hybrid-Pi model is only valid under small-signal conditions. Exactly what do we imply by small-signal is shown below.

Approximate relationship between I<sub>C</sub> and V<sub>BE</sub>:  $I_C \cong I_S \exp\left(\frac{V_{BE}}{V_T}\right)$  (BJT under active region)

Say 
$$V_{BE} \rightarrow V_{BE} + \Delta V_{BE} \longrightarrow I_C' = I_S \exp\left(\frac{V_{BE} + \Delta V_{BE}}{V_T}\right) = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \exp\left(\frac{\Delta V_{BE}}{V_T}\right)$$

Upon using Taylor's expansion:

$$I_{C}' = I_{C} \exp\left(\frac{\Delta V_{BE}}{V_{T}}\right) = I_{C} \left(1 + \frac{\Delta V_{BE}}{V_{T}} + \frac{1}{2} \left(\frac{\Delta V_{BE}}{V_{T}}\right)^{2} + \frac{1}{6} \left(\frac{\Delta V_{BE}}{V_{T}}\right)^{3} + \dots\right)$$

Let :  $i_C = I_C' - I_C = \Delta I_C$   $\Delta V_{BE} = v_{B'E} << V_T$  These higher-order terms (HOT) are ignored

Then: 
$$i_C = \Delta I_C \cong \frac{I_C}{V_T} v_{B'E} = g_m v_{B'E}$$
 
$$g_m = \frac{dI_C}{dV_{BE}} \cong \frac{i_C}{v_{BE}} = \frac{I_C}{V_T}$$

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### 2

# Conditions When Hybrid-Pi Model Can Be Applied

- 1. Only valid for small-signal operation, not valid for power amplifier.
- 2. Extra conditions:
  - $\bullet$  h<sub>fe</sub> close to h<sub>FE</sub> (small-signal current gain similar to large-signal current gain).
  - $\bullet \ \Delta V_{BE} = v_{B'E} << V_T$

See the book by Millman & Halkias [5], Gray & Meyer [4] for further information.

Example

Assuming  $\Delta V_{BE}$  <<  $V_{T}$  implies  $\Delta V_{BE}$  < 0.1 $V_{T}$ .  $\Delta V_{BE}$  must be smaller than 2.6mV for the hybrid pi model to be accurate.

$$k = 1.381 \times 10^{-23} JK^{-1}$$

$$T = 300K \text{ (about } 27^{\circ} C\text{)}$$

$$q = 1.602 \times 10^{-19} C$$

$$V_T = \frac{kT}{q} \cong 0.0259V \cong 26mV$$

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

# Useful BJT Figure of Merit (1) - The Transition Frequency $(f_T)$

- The transition frequency,  $f_T$  is the frequency where the small signal current gain  $i_o/i_s$  of the circuit approaches unity.
- It is dependent on the small signal capacitance C<sub>e</sub> and C<sub>c</sub>.

- Beyond  $f_T$ , a transistor is useless as an amplifier (for both current and voltage amplification). Hence  $f_T$  fixes the upper usable frequency of a BJT device.
- $f_T$  is a function of D.C. condition,  $f_T(I_C, V_{CE})$ , can you explain why?

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

20

## Useful BJT Figure of Merit (2) – The f<sub>max</sub>

- Another useful figure of merit is the maximum frequency of oscillation, f<sub>max</sub>.
- This is the maximum frequency where the transistor circuit, with output connected to the input (with appropriate impedance matching network), oscillates.
- Typically f<sub>max</sub> > f<sub>T</sub>.
- f<sub>max</sub> corresponds to the frequency where maximum available power gain (G<sub>amax</sub>) of the transistor equals to 1.

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### PN Junction Capacitance and the Base **Transit Time**

- The PN junction capacitance can be written as  $C_X = C_{DX} + C_{TX}$  for BC and BE junction, x = C or E.
- $C_{DX}$  is the diffusion capacitance while  $C_{TX}$  is the depletion region capacitance (also called the space charge capacitance).
- $C_{\mathrm{DX}}$  is negligible when the PN junction is reverse biased and is the dominant capacitance when the PN junction is forward biased.
- Thus for a BJT operating in Active Region,  $C_E \approx C_{DE}$  and  $C_C \approx C_{TC}$ .
- Where  $C_{\text{DE}}$  =  $\tau_{\text{F}}$   $g_{\text{m}}$  and  $C_{\text{TC}}$  is given by:

$$C_{TX} \cong \frac{C_{jx}}{\left(1 - \frac{V_{BX}}{V_{jX}}\right)^m} \quad x = C \text{ or } E$$

- $\tau_{\rm F}$  is the base transit time (the average life time of minority charge carrier in base - for NPN transistor this is the average life time of electrons in the Base before being 'sucked' into the Collector region).
- $C_{ix}$  is the depletion region capacitance when  $V_{BX}$ =0 and  $\emph{m}$  and  $V_{jx}$  are parameters usually determined empirically from measurement. A smaller  $\tau_F$  will yield a larger  $f_T$ .

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### More on PN Junction Capacitance (1)

The diffusion capacitance is given by (see Chapter 3, [5], chargecontrol description of a PN junction):



- $I_{hpn}$  is the current component due to injection of holes from P to N region, while I<sub>enp</sub> is the component from injection of electrons from N to P region. Together they constitute the forward biased current I<sub>F</sub>.
- Similarly under reverse biased the diffusion capacitance is given by:





Since  $I_{epn}$  and  $I_{hnp}$  are extremely small,  $C_{D}$  is also very small (<10<sup>-13</sup> typical).


© 2012-2016 by Fabian Kung Wai Lee

 
#### **More on PN Junction Capacitance (2)**

- For a typical NPN transistor, the N-type region of the Emitter is highly doped and P-type region of the Base is lightly doped.
- Thus under forward biased (BE junction forward biased),  $I_{hpn} << I_{enp}$ ,  $I_{E} \cong I_{epn}$ . And  $C_{DE}$  can be approximated as:  $C_{DE} \cong \frac{\tau_e I_{enp}}{c_{DE}} \cong \frac{\tau_e I_E}{c_{DE}} \cong \frac{\tau_e$
- Recognizing that  $\tau_{\rm F} = \tau_{\rm e}$   $C_{DE} \cong \frac{\tau_F I_C}{\eta V_T} = g_m \tau_F$
- A plot of C<sub>T</sub> versus junction voltage is shown below (see Chapter 1, [4]). Again charge-control description of a PN junction is used to derive the capacitance.



 

 

 

#### **MOSFET and MESFET (2)**



- For operating frequency > 2GHz, FET are usually used in place of BJT in microwave circuits. Typically MESFET is used in both discrete and integrated circuit form, while MOSFET is only used in integrated circuit.
- Among BJT, MOSFET and MESFET, MESFET has the highest transition frequency f<sub>T</sub> and is often used for high-performance RF/microwave circuits:
- (1) FET has better noise characteristic (lower noise figure).
- (2) FET such as MESFET can be constructed from compound semiconductor such as Gallium Arsenide (GaAs) (the so-called III-V compound) which has higher electron mobility than Silicon.
- (3) Smaller Gate capacitance in MESFET structure. The Schottky barrier (Metal-Semiconductor contact) on the Gate of MESFET has smaller capacitance as compared to the gate oxide capacitance of MOSFET, the PN junction in JFET or the C<sub>π</sub> of BJT.
- (4) Also ohmic contact on the Drain and Source on MESFET reduces the corresponding Drain and Source capacitance.
- (2), (3) and (4) contributed to much higher f<sub>T</sub> in MESFET.

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee


37

#### **Small-Signal Model for FET** $C_{gd}$ $r_D$ D $G_m v_{in}$ Thus you can see that for small-signal or $\mathsf{r}_{\mathsf{S}}$ A.C. equivalent circuit, BJT and FET are more or S less equivalent. Causes reduction of voltage and current gain at high frequency Chapter 6 (November 2016) 38 © 2012-2016 by Fabian Kung Wai Lee
 
#### **HBT and HEMT (1)**



- Most modern high-performance RF/microwave circuits employ FET, for instance GaAs (Gallium Arsenide) MESFET for operating frequency > 3GHz. GaAs MESFET can operate in excess of 10GHz.
- Since late 1990s, Hetero-junction Bipolar Transistor (HBT) is introduced commercially. In HBT different semiconductor material is used for the Base, Emitter and Collector region. For instance P-type GaAs for Base, N-type GaAs for Collector and N-type AlGaAs for Emitter. Another example of HBT is the SiGe (Silicon-Germanium) on Silicon process. Here a compound of SiGe is used for the Base. An example of discrete SiGe HBT is BFP620 from Infineon Technologies (www.infineon.com) with f<sub>T</sub> of 65GHz!



Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### **HBT and HEMT (2)**



- The hetero-junction structure results in valence band discontinuity between the Base and Emitter of an NPN structure [7].
- This discontinuity reduces the injection of holes from Base to the Emitter, while allowing the injection of electron from Emitter to Base. This effect improves emitter efficiency ( $\gamma$ ).
- The emitter efficiency is further improved by being able to construct a transistor with heavily doped and very thin Base region, thus basespreading resistance  $(r_{b'b})$  and base-transit time  $(\tau_F)$  are reduced.
- Smaller  $\tau_F$  results in smaller  $C_e$ .  $f_T \cong \frac{1}{2\pi} \frac{g_m}{C_a + C_C}$

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### **HBT and HEMT (3)**



- Hetero-junction approach is also applied to MESFET, in the channel region of the FET, called Modulation-Doped Field Effect Transistor (MODFET) [7].
- However since FET operation does not depend on charge injection, but
  of charge transport in the channel between the Drain and Source
  terminals, the introduction of hetero-junction structure in the channel
  serves to increase the electron mobility, allowing very rapid exchange of
  electrical signal between Drain and Source. This improves the f<sub>T</sub> of the
  FET.
- Although based on MODFET approach, the resulting FET is usually called **High Electron Mobility Transistor (HEMT)**. Higher electron mobility allows the device to response to rapid changes in its Gate. Effectively this reduces  $C_{\alpha s}$ .
- Such transistor can operate well into the millimeter wave region or in excess of 100GHz.


Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

41
 
# HBT and HEMT (4)

An example of HEMT using GaAs as the substrate.



Usually in depletion mode. But can be designed to work in both depletion and enhancement mode

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee



- Since 2006, the CMOS technology, where the main active component is the MOSFET, is also used extensively for applications up to a few GHz. This is usually implemented in integrated circuit form.
- For all these active devices, the small-signal equivalent are almost similar to the hybrid-pi model of the BJT, so in this course we only concentrate on RF circuit design using BJT. The major difference is in the way we bias the active devices. FET active devices, which come in enhancement and depletion mode will require different biasing circuits.
- Also depletion mode device sometimes requires negative d.c. supply.
- Refer to Roberson & Lucyszyn [3], Gilmore & Besser (Vol. II) [8] for more information. More advanced and updated information can also be obtained from Sze [7].

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

4

# 2.0 Review of BJT Amplifier Biasing and S-Parameters Computation


Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee
 
#### D.C. Biasing for BJT and FET (1)

- Biasing means putting proper d.c. voltages and currents at a transistor terminals (Collector, Base, Emitter) so that the device is in the required operating region, when no a.c. signal is applied.
- A bipolar junction transistor (BJT) has 4 operating regions: Active, Cutoff, Saturation and Inverse.
- For small-signal amplifier, we bias the transistor in the Active region.
- Small-signal amplifiers is usually of type Class-A, because it needs to have linear response.

Key point of BJT biasing for small-signal operation, NPN transistor: V<sub>C</sub>>V<sub>B</sub>>V<sub>E</sub> (Active region)



Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### D.C. Biasing for BJT and FET (2)

- For <u>large-signal amplifier</u>, we may bias the transistor in the Active and the Cut-off regions, depending on the Class of the amplifier.
- Biasing also applies to field effect transistor (FET), which has 4 distinct operating regions: Active (also called Saturation), Linear, Cut-off and Inverse.
- · Small-signal FET amplifier is usually biased in Active region.
- Large-signal FET amplifier can be biased in Active and Cut-off regions.

Key point of FET biasing for small-signal operation, N-channel:

V<sub>D</sub> > V<sub>G</sub> > V<sub>S</sub> (Active region)

V<sub>DS</sub> > V<sub>GS</sub> - V<sub>TN</sub>

Threshold voltage

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

46

 $I_{B4}$ 

 $I_{B3}$ 


45

 $I_{\rm B2}$ 

 $I_{R1}$ 
 
#### **BJT Amplifier Configurations**


- A transistor is a 3 terminals device. Thus 2 of the terminals can be used to for signal input and output. The third terminal can be grounded, usually A.C. grounded with respect to the other terminals.
- This grounded terminal is thus called the common terminal, and hence the name for transistor amplifier configuration.



Note that a similar situation exist for FET amplifier, we call these Common-Source, Common-Drain and Common-Gate FET amplifiers

© 2012-2016 by Fabian Kung Wai Lee

 **Typical D.C. Biasing Circuits for BJT** 



•24

# Typical D.C. Biasing Circuits for BJT (2)

• Bypass or decoupling capacitors are used to stabilize the d.c. voltage and current levels and to isolate RF signals from other circuitry.


Sometimes these capacitors can be put right after the RF choke to improve their effectiveness.


To shunt out RF power that leaks from RF choke


Input

 $= R_{b2}$   $= R_{e}$   $C_{e}$ Chapter 6 (November 2016) © 2012-2016 by Fabian Kung Wai Lee 49

Output

 


 

 
 
# Typical D.C. Biasing Circuits for BJT (6)

• Active Bias (suitable for low frequency to microwave band):




Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

5
 
# Typical D.C. Biasing Circuits for BJT (7)

Another form of Active Bias using current mirror, popular for high power application with large Collector current I<sub>C</sub>. Usually I<sub>C</sub> >> I<sub>ref</sub>.



Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### Some Issues Concerning D.C. Biasing

- Biasing network must not interfere with the flow of RF energy during normal operation. Hence the quality of the bypass capacitors and RF chokes is vital.
- Temperature stability. Bias point or quiescent point (i.e. I<sub>C</sub>, V<sub>CE</sub>) of the BJT must not change a lot with temperature variation, to ensure that the performance of the active circuit is not affected by temperature variation. In this sense, active bias is the most stable, followed by Emitter bias and voltage feedback bias.
- Compensation for temperature variation using diode in Emitter bias is available, for instance see Millman & Halkias [5].
- Stability against parameters variation of the BJT. Again active bias and emitter feedback bias are less susceptible, followed by base feedback bias and collector feedback bias. See Milman & Halkias [5] for analysis.


Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

5
 
#### **FET Amplifier Biasing**

- Due to time constraint we will not focus on field-effect transistor (FET).
- However it needs to be mentioned that the FET amplifier can also be classified into Common-Source (CS), Common-Gate (CG) and Common-Drain (CD).
- The DC biasing circuit discussed can also be modified to accommodate FET based active device. Again for RF/microwave circuits typically Nchannel device is used.




Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee
 
#### **Example 2.1 - BJT Amplifier Biasing** and Small-Signal Equivalent Circuit

- Determine the quiescent point (Q) of the transistor and its D.C. stability. Given  $h_{FE(min)} = 100, h_{FE(max)} = 200.$
- Derive the approximate small-signal equivalent circuit of the following amplifier schematic. Use hybrid pi model for the BJT. Given  $V_A$ =74.03V,  $C_{jc}$ =3.638pF,  $C_{je}$ =4.493pF,  $r_{b'b}$ =10,  $h_{fe}$ =300,  $V_{jc}$ =0.75, m=0.3085,  $\tau_{F}$ = 301.2pS.
- If the circuit is going to be used at 430MHz, suggest suitable values for C<sub>c1</sub>, C<sub>c2</sub>, C<sub>e</sub> and the required RF choke inductance.
- Finally suggest suitable value for C<sub>d</sub>.




Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### **Example 2.1 Solution**

#### (1) DC Analysis:

 

 $V_B \cong \frac{4.7}{4.7+10} \cdot 5 = 1.60V$ Assuming  $h_{FE}$  is large,  $I_1 >> I_B$ .

Assuming transistor is in active  $I_C$  region,  $V_{BE} = 0.6V$ .

 $V_E = V_B - 0.6 = 1.00V_{\text{x}}$ 

Using Ohm's Law:

 $I_E = \frac{V_E}{220} = 4.545 m Å$  V<sub>CE</sub> and I<sub>C</sub> constitute the Q point

Assuming  $h_{FE}$  is large,  $I_C >> I_B$ .

 $I_E = I_C + I_B \cong I_C$  $\Rightarrow I_C \cong 4.545 mA$ 

Using Kirchoff's Voltage Law:  $V_C = V_{cc} - 470 \cdot I_C = 2.864V$ 

Verify that transistor is under Active Region:

$$V_{BC} = V_B - V_C = 1.6 - 2.864 = -1.264V$$

Thus BC junction is reverse biased. And in previous slide it has been shown that BE junction is forward biased, so the transistor is biased in Active Region, the circuit is destined for Class A operation.

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### **Example 2.1 Solution Cont...**

(2) D.c. biasing stability analysis (Stability Factor)

(see derivation in Chapter 9 of Millman & Halkias [5]): 
$$\frac{\partial I_C}{\partial I_{CO}} = (1 + h_{FE}) \frac{1 + R_b / R_e}{1 + h_{FE} + R_b / R_e} = (1 + 150) \frac{1 + 3197}{1 + 150 + 3197} = 14.17$$

$$R_b = \frac{R_{b1}R_{b2}}{R_{b1} + R_{b2}} \cong 3197 \quad , \text{ use } h_{FE} = \frac{1}{2} \left( h_{FE}(\max) + h_{FE}(\min) \right) = 150$$

$$R_{b1}+R_{b2}$$

Variation of I<sub>c</sub> when I<sub>co</sub> changes

$$\frac{\partial I_c}{\partial V_{BE}} = \frac{-h_{FE} / R_e}{1 + h_{FE} + R_b / R_e} = \frac{-150 / 220}{1 + 150 + 3197} = -0.0042$$

Variation of  $I_c$  when  $V_{\text{BE}}$  changes due to temperature change

$$\frac{\partial I_{\mathcal{C}}}{\partial h_{FE}} \approx \frac{\left(I_{\mathcal{C}}\big|_{h_{FE} = h_{FE}\left(\text{min}\right)}\right) \cdot \left(\frac{\partial I_{\mathcal{C}}}{\partial I_{\mathcal{C}O}}\big|_{h_{FE} = h_{FE}\left(\text{max}\right)}\right)}{h_{FE}\left(\text{min}\right) \left(1 + h_{FE}\left(\text{max}\right)\right)} \approx \frac{0.00454 \cdot 14.486}{100(1 + 200)} = 3.272 \times 10^{-6}$$

Variation of I<sub>c</sub> due to device parameter variation

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### **Example 2.1 Solution Cont...**

(3) Deriving small-signal Hybrid-Pi model parameters:

$$g_m \approx \frac{I_C}{26} = \frac{4.545}{26} = 0.1748\Omega^{-1}$$
 $r_{b'e} = \frac{h_{fe}}{g_m} = 1.682k\Omega$ 
 $r_{ce} = \frac{V_A}{I_C} = 16.288k\Omega$ 

 $r_{b'c} = h_{fe}r_{ce} = 4.886 \,\mathrm{M}\Omega$  Can be ignored, considered open circuit

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee


#### **Example 2.1 Solution Cont...**

Since BE junction is forward biased:

$$C_E = C_{DE} + C_{TE} \cong C_{DE}$$
  
 $\Rightarrow C_E \cong \tau_F \ g_m = 53.734 \ pF$ 

Since BC junction is reverse biased:
 
$$C_C = C_{DC} + C_{TC} \cong C_{TC} = \frac{C_{jc}}{\left(1 - \frac{V_{BC}}{V_{jc}}\right)^m} = \frac{3.638 \times 10^{-12}}{\left(1 - \frac{-1.264}{0.75}\right)^{0.3085}} = 2.682 \, pF$$



Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### **Example 2.1 Solution Cont...**

(4) Finding the values of coupling capacitors, bypass capacitor and RF choke.

Typically, values of  $L_1$ ,  $L_2$  and  $L_3$  should be chosen such that the reactance of the inductors is greater than 1000 at the operating frequency. The values  $C_{c1}$ ,  $C_{c2}$  and  $C_e$  are chosen such that the reactance of the capacitors is less than 1 at the operating frequency. Care must be taken to ensure that the actual component self-resonance frequency be at least 50% higher than


$$\begin{aligned} |Z_L| &= 2\pi J L > 1000 \\ \Rightarrow L &> \frac{1000}{2\pi (430 \times 10^6)} = 370.128 nH \\ |Z_C| &= \frac{1}{2\pi J C} < 1 \\ \Rightarrow C &> \frac{1}{2\pi (430 \times 10^6)} = 370.128 pF \end{aligned}$$

- Thus we can use 390nH (standard value) for  $L_1$ ,  $L_2$  and  $L_3$ . Make sure that the self-resonance frequency and Q-factor of the chosen practical inductor is sufficient for this purpose.
- Similarly 390pF is chosen for  $C_{c1}$ ,  $C_{c2}$  and  $C_{e}$ .

Chapter 6 (November 2016)


the operating frequency.

© 2012-2016 by Fabian Kung Wai Lee

 



 - We would like to find out how the circuit will behave if a sinusoidal voltage of certain frequency is injected into it's input.
- It is reasonable to expect that the amplifier circuit to behave differently at different frequencies.
- Of interest is the ratio of the various voltages and currents on the terminals of the basic amplifier circuit, i.e. the classical parameters.



•32

#### **Summary of Amplifier Parameters Based on Configurations**

The voltage gain, current gain, input and output impedance of CE, CC and CB transistor amplifier configurations are summarized here ([4], [5]), similar conclusions can be derived for FET based amplifiers.

Amplifier configuration	Voltage Gain	Current Gain	Input Impedance	Output Impedance	Phase Output/Input Voltage	Linearity
CE	High	High	Moderately high	Moderately low	180°	Moderate
СС	≅ 1	High	High	Low	0°	Moderate
СВ	High	≅ 1	Low	High	0°	High

Each configuration has it uses, for instance CE type amplifier is usually used for general purpose amplifier. CC is good for buffer or isolation. CB is typically used in multi-stage amplifiers and oscillators, and for lowfrequency operation, CB can be used as current source for its high output impedance. Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

#### **Two-Stage Amplifiers**

- Here we only focus on single-stage amplifier.
- However we would like to mention that two-stages amplifiers are also very important, as they can combine the individual benefits of singlestage amplifiers.
- Example of popular two-stages amplifiers are CE-CB (cascade, for high linearity and high voltage gain), CC-CC (Darlington pair), CE-CE (for high power gain), CE-CC (to drive high current load or power gain).
- The FET equivalent will be CS-CG, CD-CD, CS-CS and CS-CD.

Chapter 6 (November 2016)


© 2012-2016 by Fabian Kung Wai Lee

## Characterizing the Frequency Response of the Amplifier Circuit at RF/Microwave Band


- For amplifier operating at RF and microwave frequencies, a more convenient set of parameters are the S-parameters.
- The amplifier is considered as a 2-port network, and the S-parameters
   s<sub>11</sub>, s<sub>12</sub>, s<sub>21</sub> and s<sub>22</sub> can be measured or derived. Bear in mind here that
   we assume the amplifier to be linear or small-signal.
- S-parameters can be reliably measured at RF and microwave frequencies using instrument called **Vector Network Analyzer** or derived from linear circuit analysis.
- Instead of dealing with absolute voltage and current phasors, Sparameters deal with the ratio of incident and reflected waves. This is
  based on the fact that high frequency amplifier can be connected to
  transmission lines/waveguides at both its terminals. Of course in the
  extreme case the transmission line can be so short that it vanishes.
- The next slide shows how S-parameters are obtained. For more information please refer to the notes of RF Circuit Design – Passive Circuit.

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

 

 
# Example 2.2 – Computing SParameters from Circuit Simulator • Here is a screen shot of the schematic drawn using Agilent's Advanced Design System (ADS) software. Setting up small-signal S-parameters computation in a commercial simulator Chapter 6 (November 2016) Setting up small-signal SSetting up small-signal


 
#### Example 2.3 – Obtaining Small-Signal S-Parameters for BJT Amplifier Analytically

 Consider the circuit of Example 2.1 being terminated with source and load impedance of R<sub>o</sub>. Ignoring the package parasitic, the small-signal equivalent circuit is as shown below.



#### **Example 2.3 Solution**



Using Nodal Analysis...

Node 1: 
$$\frac{V_1 - V_3}{R_2} + \frac{V_1}{R_1} = \frac{V_S}{R_O}$$
 Let  $G_2 = \frac{1}{R_2}$ ,  $G_1 = \frac{1}{R_1}$ ,  $Y_3 = \frac{1}{Z_3}$ ,  $G_5 = \frac{1}{R_5}$ ,  $I_s = \frac{V_S}{R_O}$   $\Rightarrow V_1(G_1 + G_2) - G_2V_3 = I_S$  (1)

Node 3: 
$$G_2(V_3 - V_1) + Y_4(V_3 - V_2) + Y_3V_3 = 0$$
  

$$\Rightarrow -G_2V_1 - Y_4V_2 + (G_2 + Y_3)V_3 = 0$$
 (2)

Node 2: 
$$Y_4(V_2 - V_3) + g_m V_3 + G_5 V_2 = 0$$
  
 $\Rightarrow (Y_4 + G_5)V_2 + (g_m - Y_4)V_3 = 0$  (3)

From (1): 
$$V_1 = \frac{I_s + G_2 V_3}{G_1 + G_2}$$
 (4)

From (2): 
$$V_2 = \frac{Y_4 - g_m}{Y_4 + G_5} V_3$$
 (5)

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee



Extra

Putting (4) & (5) into (2): 
$$-G_2\left(\frac{I_S+G_2V_3}{G_1+G_2}\right) - Y_4\left(\frac{Y_4-g_m}{Y_4+G_5}\right)V_3 + (G_2+Y_3)V_3 = 0$$

$$\Rightarrow V_3 = \frac{\frac{G_2I_S}{G_1+G_2}}{G_2+Y_3-\left(\frac{G_2^2}{G_1+G_2}\right)-\left(\frac{Y_4^2-Y_4g_m}{Y_4+G_5}\right)}$$
(6)

Using (4): 
$$V_{1} = \frac{I_{s}}{G_{1} + G_{2}} \left[ \frac{\frac{G_{2}}{G_{1} + G_{2}} \cdot G_{2}}{G_{2} + Y_{3} - \left(\frac{G_{2}^{2}}{G_{1} + G_{2}}\right) - \left(\frac{Y_{4}^{2} + Y_{4}g_{m}}{Y_{4} + G_{5}}\right)} \right]$$

$$\Rightarrow V_1 = \frac{V_S}{R_O(G_1 + G_2)} \left[ 1 + \frac{G_2^2}{G_1 G_2 + G_1 Y_3 + G_2 Y_3 - Y_4 (G_1 + G_2) \left( \frac{Y_4 - g_m}{Y_4 + G_5} \right)} \right]$$
 (7)

Using (5): 
$$V_{2} = \left(\frac{Y_{4} - g_{m}}{Y_{4} + G_{5}}\right) \frac{G_{2}V_{s}}{R_{o}\left[G_{1}G_{2} + G_{1}Y_{3} + G_{2}Y_{3} - Y_{4}\left(G_{1} + G_{2}\left(\frac{Y_{4} - g_{m}}{Y_{4} + G_{5}}\right)\right)\right]}$$
(8)

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

7

### **Example 2.3 Solution Cont...**



$$I_1 = \frac{V_S - V_1}{R_0}$$
 (9)

$$I_2 = \frac{-V_2}{R_2}$$
 (10)

Using the relationship between port voltage, current and the normalized voltage waves in S-parameter theory (see Chapter 2):

$$a_1 = \frac{1}{2\sqrt{R_o}} (V_1 + R_o I_1) = \frac{1}{2\sqrt{R_o}} V_s$$
 From (9)

$$b_1 = \frac{1}{2\sqrt{R_o}} (V_1 - R_o I_1) = \frac{1}{2\sqrt{R_o}} (2V_1 - V_s)$$

$$b_2 = \frac{1}{2\sqrt{R_o}} (V_2 - R_o I_2) = \frac{1}{2\sqrt{R_o}} (2V_2) = \frac{V_2}{\sqrt{R_o}}$$

$$a_2 = 0$$

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

- 7

#### **Example 2.3 Solution Cont...**



#### Hence:

$$\begin{split} S_{11} &= \frac{b_1}{a_1} \bigg|_{a_2 = 0} = \frac{2V_1 - V_s}{V_s} = 2\frac{V_1}{V_s} - 1 \\ &\Rightarrow S_{11} = \left(\frac{2}{R_o(G_1 + G_2)}\right) \left(1 + \frac{G_2^2}{G_1G_2 + G_1Y_3 + G_2Y_3 - Y_4(G_1 + G_2)\left(\frac{Y_4 - g_m}{Y_4 + G_5}\right)}\right) - 1 \\ S_{21} &= \frac{b_2}{a_1} \bigg|_{a_2 = 0} = \frac{2V_2}{V_s} \\ &\Rightarrow S_{21} = \left(\frac{Y_4 - g_m}{Y_4 + G_5}\right) \left(\frac{2G_2}{R_o\left(G_1G_2 + G_1Y_3 + G_2Y_3 - Y_4(G_1 + G_2)\left(\frac{Y_4 - g_m}{Y_4 + G_5}\right)\right)}\right) \end{split}$$

By injecting the source at output we can obtain expression for  $s_{22}$  and  $s_{12}$ . This is the procedure used by most CAD tools to obtain S-parameters for linear circuits.


Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

7
 
# Example 2.4 – A Transistor Biasing Circuit in Integrated Circuit (IC)

 Here is an example of a active biasing for a power amplifier circuit. The transistor on the right is a RF power transistor. This is an example of active biasing using a Current Mirror [4].



Class-A/AB Single power cell unit block: 1 power HBT (2umx20um emitter, 2 fingers) using TFR resistors with Stack coupling capacitors.

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

# Appendix 1 Some Do-It-Yourself (DIY) Active RF Circuits

Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee


77

#### **UHF Low-Noise Amplifier**

Supply: 3.0-4.0V


Bandwidth: 850-910 MHz

 Transducer Power Gain (G<sub>T</sub>): 11-12 dB Noise Figure (F): < 1.45




Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

 

#### 2.2-2.6 GHz Microwave Voltage-Controlled Oscillator (VCO)

  Example of microwave oscillator prototype, built on 0.8 mm thick Rogers 4350 substrate with top and bottom side copper.



Chapter 6 (November 2016)

© 2012-2016 by Fabian Kung Wai Lee

# 400 to 550 MHz UHF Frequency Synthesizer Prototype

This is a low-cost frequency synthesizer using a digital phase-locked loop PLL integrated circuit from National Semiconductor, LMX2306 (now obsoleted).

The voltage controlled oscillator (VCO) is designed using techniques presented in this course.

